

# **Introduction to Boole algebra**

Binary algebra

# Boole algebra


- George Boole's book released in 1847
- We have only two digits: true and false
- We have NOT, AND, OR, XOR etc operations
- We have axioms and theorems
- In computers represented by bits 1 and 0
- In circuits LOW and HIGH voltages
- Operations implemented in hardware as gates or more precisely as certain configuration of transistors

# Boole operations

AND, OR, XOR etc
 
# Conjunction (AND)

- True if both operands are true
- Scientific:  $A \wedge B$
- Alternatively:  $A . B$
- C/Java:  $A \&\& B$
- Python:  $A \text{ and } B$
- Bitwise:  $A \& B$




| A | B | Output |
|---|---|--------|
| 0 | 0 | 0      |
| 0 | 1 | 0      |
| 1 | 0 | 0      |
| 1 | 1 | 1      |

# Disjunction (OR)

- True if at least one of the operands is true
- Scientific:  $A \vee B$
- Alternatively:  $A + B$
- C/Java:  $A \parallel B$
- Python:  $A \text{ or } B$
- Bitwise:  $A \mid B$


*2-input OR gate*

 

| A | B | Output |
|---|---|--------|
| 0 | 0 | 0      |
| 0 | 1 | 1      |
| 1 | 0 | 1      |
| 1 | 1 | 1      |
 
# Negation (NOT)

- True if and only if A is false
- Scientific:  $\neg A$
- C/Java: `!A`
- Python: `not A`
- Bitwise: `~A`



| Input | Output |
|-------|--------|
| 1     | 0      |
| 0     | 1      |

# Exclusive OR (XOR)

- True if and only if A and B are unequal
- Scientific:  $A \nabla B$
- Alternatively:  $A \oplus B$
- Bitwise XOR in Python/C/Java:  $A \wedge B$

*Exclusive-OR gate*




| A | B | Output |
|---|---|--------|
| 0 | 0 | 0      |
| 0 | 1 | 1      |
| 1 | 0 | 1      |
| 1 | 1 | 0      |

# Negated AND (NAND)

- Output of AND gate is negated
- Commonly written as:


$$\overline{A \cdot B} \text{ or } A \uparrow B$$

*2-input NAND gate*

 

| A | B | Output |
|---|---|--------|
| 0 | 0 | 1      |
| 0 | 1 | 1      |
| 1 | 0 | 1      |
| 1 | 1 | 0      |

*Equivalent gate circuit*

 




# Negated OR (NOR)

- Output of OR gate is negated
- Commonly written as:


$$\overline{A + B} \text{ or } A - B$$

*2-input NOR gate*

 

| A | B | Output |
|---|---|--------|
| 0 | 0 | 1      |
| 0 | 1 | 0      |
| 1 | 0 | 0      |
| 1 | 1 | 0      |

*Equivalent gate circuit*

 

# Axioms and theorems

- Identity:
  - $X \text{ OR } 0 = X$
  - $X \text{ AND } 1 = X$
- Null:
  - $X \text{ OR } 1 = 1$
  - $X \text{ AND } 0 = 0$
- Idempotency:
  - $X \text{ AND } X = X$
  - $X \text{ OR } X = X$

# Axioms and theorems

- Involution:  $\text{NOT NOT } X = X$
- Complementarity:
  - $X \text{ OR NOT } X = 1$
  - $X \text{ AND NOT } X = 0$
- Commutativity:
  - $X \text{ OR } Y = Y \text{ OR } X$
  - $X \text{ AND } Y = Y \text{ AND } X$

# Axioms and theorems

- Distributivity:
  - $X \text{ AND } (Y \text{ OR } Z) = X \text{ AND } Y \text{ OR } X \text{ AND } Z$
  - $X \text{ OR } (Y \text{ AND } Z) = X \text{ AND } Y \text{ OR } X \text{ AND } Z$
- Uniting:
  - $X \text{ AND } Y \text{ OR } X \text{ AND NOT } Y = X$
  - $(X \text{ OR } Y) \text{ AND } (X \text{ OR NOT } Y) = X$
- And so forth

# Disjunctive normal form (DNF)

- Disjunction of clauses, where a clause is a conjunction of literals
- Simply put it's an OR of AND-s:  
 $(\text{NOT } A \text{ AND } B) \text{ OR } (A \text{ AND } B) \text{ OR } (\dots) \text{ OR } (\dots)$
- Karnaugh's map output is DNF
- Further optimizations/substitutions can be performed on DNF

# Gates in hardware


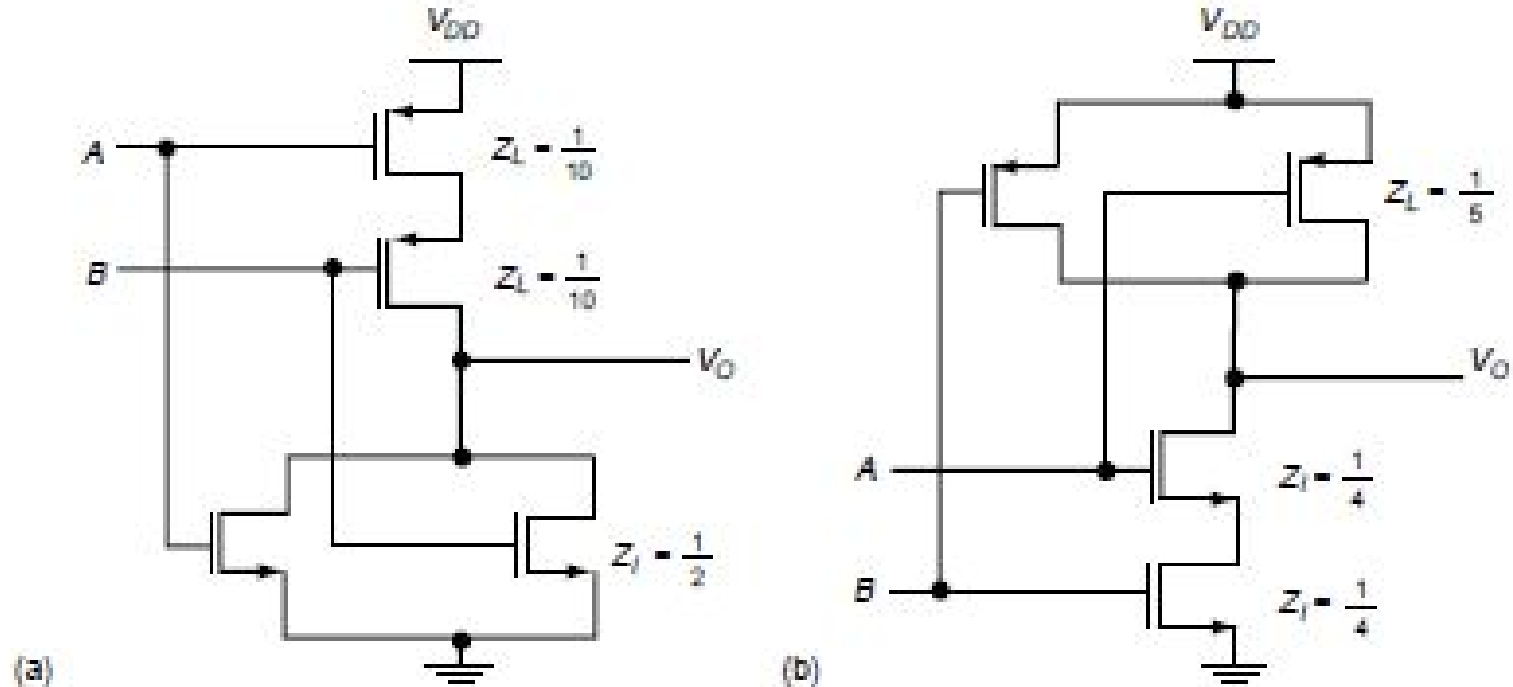
 


FIGURE 8.18 CMOS gates: (a) CMOS NOR gate, (b) CMOS NAND gate.

# NAND with CMOS

 

Latency of approximately 4ps

# **Adding in hardware**

Half adder, full adder, carry ripple adder



# Binary addition

- Essentially same as in decimal
- Bit is carried with 1+1
- How can we implement this in Boole algebra?

$$\begin{array}{r} \text{BINARY} \\ 0101 \\ + 0011 \\ \hline 1000 \end{array}$$

$$\begin{array}{r} \text{DECIMAL} \\ 5 \\ + 3 \\ \hline 8 \end{array}$$

# Half adder


| Inputs |   | Outputs |   |
|--------|---|---------|---|
| A      | B | S       | C |
| 0      | 0 | 0       | 0 |
| 1      | 0 | 1       | 0 |
| 0      | 1 | 1       | 0 |
| 1      | 1 | 0       | 1 |

Truth table

Sum = A XOR B  
Carry = A AND B



Schematic

 

Realization


Read: odd number of 1-s on inputs  
Read: both inputs are 1

# Full adder

| Input |   |     | Output |       |
|-------|---|-----|--------|-------|
| A     | B | Cin | Sum    | Carry |
| 0     | 0 | 0   | 0      | 0     |
| 0     | 0 | 1   | 1      | 0     |
| 0     | 1 | 0   | 1      | 0     |
| 0     | 1 | 1   | 0      | 1     |
| 1     | 0 | 0   | 1      | 0     |
| 1     | 0 | 1   | 0      | 1     |
| 1     | 1 | 0   | 0      | 1     |
| 1     | 1 | 1   | 1      | 1     |

Sum = A XOR B XOR Cin


Carry = (A XOR B) AND Cin OR (A AND B)

 


Read: odd number of 1-s on inputs

Read: two or more 1-s on inputs


# Full adder

 

# Full adder with NAND gates

 

# Carry ripple adder

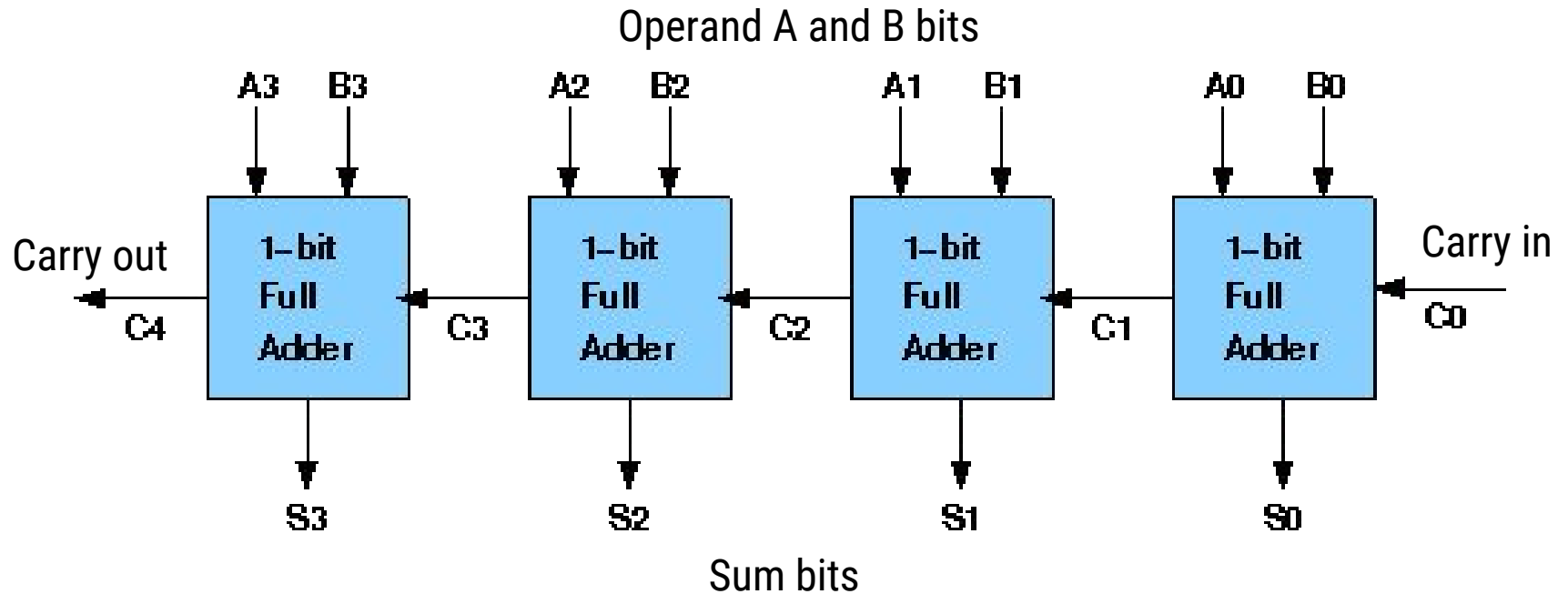

# Hitting the ceiling

- Consider clock frequency of 2GHz (500ps)
- Within one clock period we could chain up to  $500\text{ps} / 4\text{ps} \approx 125$  NAND gates in series
- Full adder carry in-carry out path contains 2 NAND gates  $500\text{ps} / 8\text{ps} \approx 62$  full adders chained
- So 64 bit *carry-ripple adder* at 2GHz is problematic if not even impossible


# Solutions

- Overclocking: Increase voltage to reduce gate delay, problem is increased thermal dissipation
- Better circuit design with less gates in critical path
- Span the operation over several processor cycles
- Law of diminishing returns can be observed



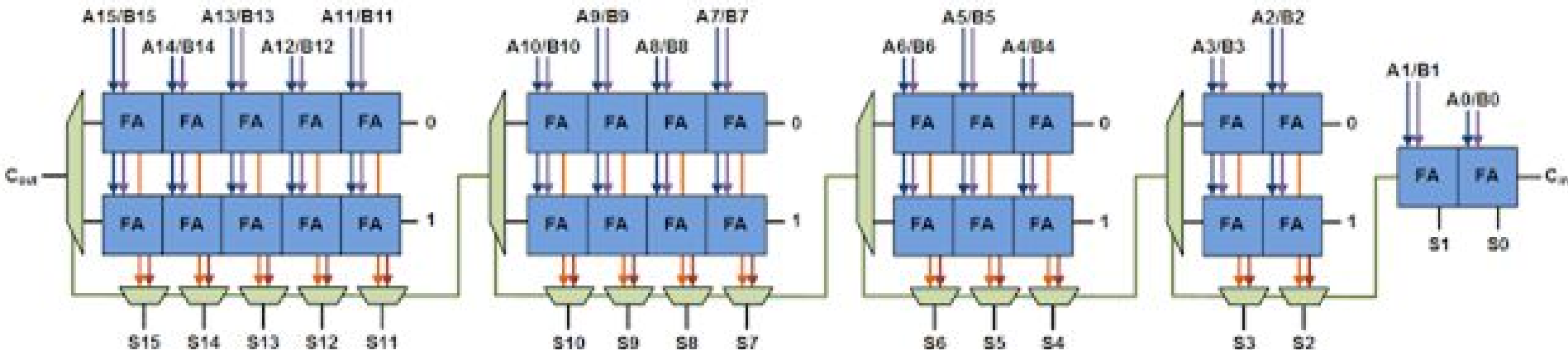
# Carry select adder

- Critical path is shorter in terms of gates
- 30 FA-s instead of 16 FA-s -> more resources used
- Mux logic



# Spanning operations

 


# Multiplexer

Selecting signals


# 2:1 multiplexer

- Selects between inputs

 



| $S$ | $I_0$ | $I_1$ | $Q_0$ |
|-----|-------|-------|-------|
| 0   | 0     | 0     | 0     |
| 0   | 0     | 1     | 0     |
| 0   | 1     | 0     | 1     |
| 0   | 1     | 1     | 1     |
| 1   | 0     | 0     | 0     |
| 1   | 0     | 1     | 1     |
| 1   | 1     | 0     | 0     |
| 1   | 1     | 1     | 1     |

# 2:1 mux with NAND gates

 
  
# 4:1 mux

- Use 2 selector inputs to select between 4 data inputs



# Multiplexer uses


- Selecting input value from registers
- Selecting result within ALU for output value
- Converting parallel data to serial
- Implementing programmable logic
  - Use input pins as programming bits
  - Use selector bits as logic inputs
  - That's basically how FPGA-s work

# Bitwise operations



# Bitwise operations


- Perform AND, OR, XOR, etc logic operation on registers
- In C/Java/Python:
  - AND:  $a \& b$
  - OR:  $a | b$
  - XOR:  $a \wedge b$

 


# Bitwise operation uses

- Overlaying sprites
- These are images or animations integrated into larger scene


First step:

 


AND

 

Second step:

 


OR

 

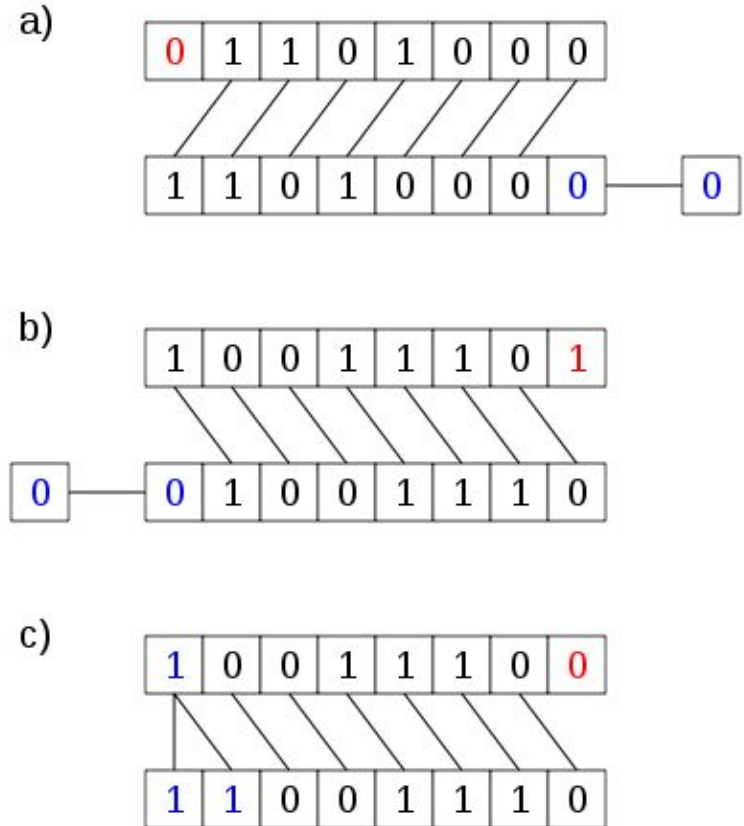
# Bit shifting

- Perform quick integer mult/div with 2 and it's powers
- In C/Java/Python
  - $x \ll y$
  - $x \gg y$
- Applied in 3D graphics


 
# Circular shift (bit rotate)


- Applied in cryptography to permutate bit sequences
- Not exposed in most programming languages, can be invoked via inlined assembly



# **ALU**


Arithmetic logic unit

# Arithmetic-logic unit

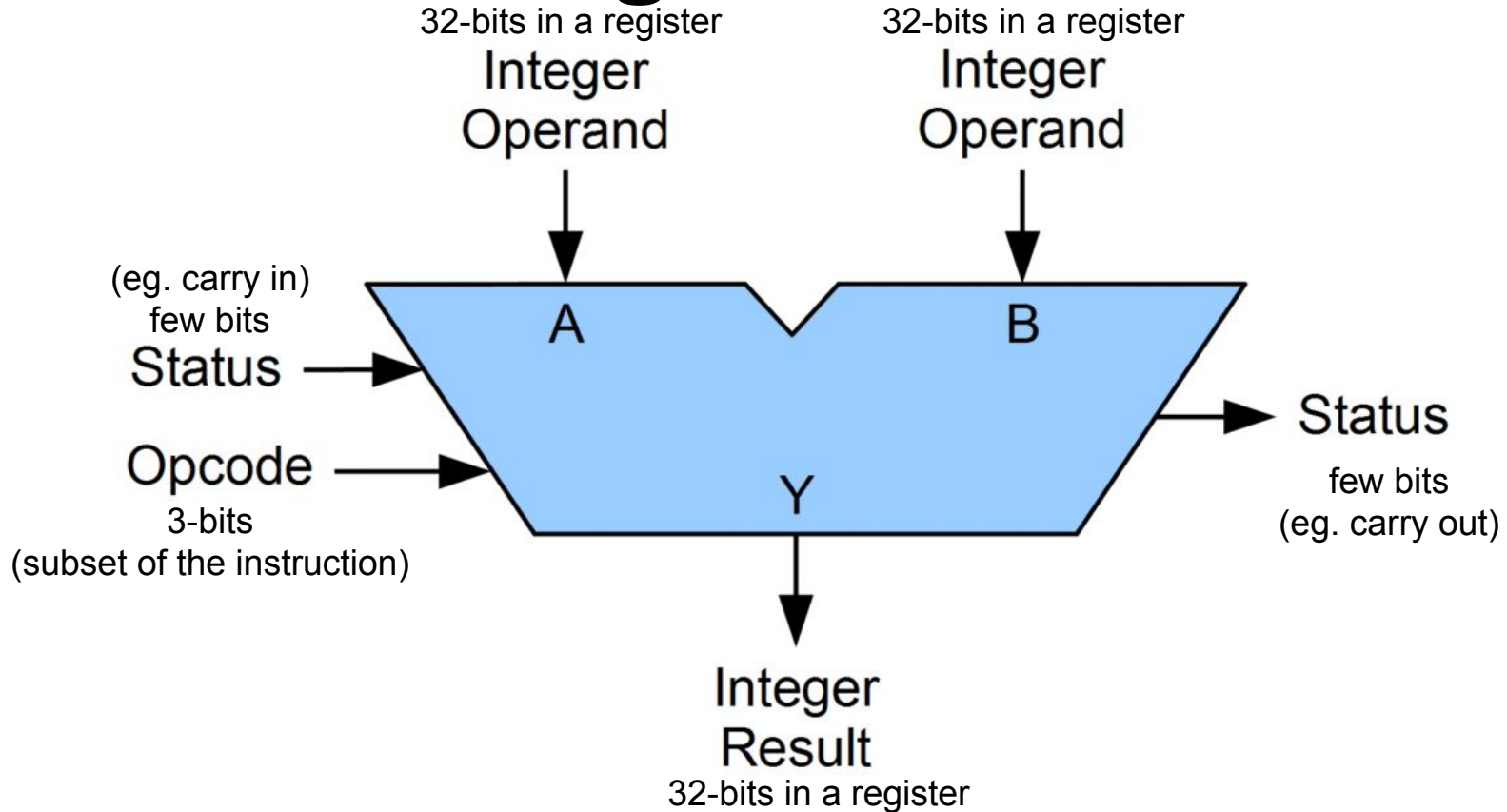
 
# Arithmetic logic unit inside

- Perform different operations
- Calculate all possible outputs
- Use multiplexer to select correct one




# ARM7 data processing opcodes

| Opcode | Mnemonic | Operation                   | Action   |
|--------|----------|-----------------------------|--|
| 0000   | AND      | Logical AND                 | $Rd := Rn \text{ AND shifter\_operand}$                              |
| 0001   | EOR      | Logical Exclusive OR        | $Rd := Rn \text{ EOR shifter\_operand}$                              |
| 0010   | SUB      | Subtract                    | $Rd := Rn - \text{shifter\_operand}$                                 |
| 0011   | RSB      | Reverse Subtract            | $Rd := \text{shifter\_operand} - Rn$                                 |
| 0100   | ADD      | Add                         | $Rd := Rn + \text{shifter\_operand}$                                 |
| 0101   | ADC      | Add with Carry              | $Rd := Rn + \text{shifter\_operand} + \text{Carry Flag}$             |
| 0110   | SBC      | Subtract with Carry         | $Rd := Rn - \text{shifter\_operand} - \text{NOT}(\text{Carry Flag})$ |
| 0111   | RSC      | Reverse Subtract with Carry | $Rd := \text{shifter\_operand} - Rn - \text{NOT}(\text{Carry Flag})$ |
| 1000   | TST      | Test                        | Update flags after $Rn \text{ AND shifter\_operand}$                 |
| 1001   | TEQ      | Test Equivalence            | Update flags after $Rn \text{ EOR shifter\_operand}$                 |
| 1010   | CMP      | Compare                     | Update flags after $Rn - \text{shifter\_operand}$                    |
| 1011   | CMN      | Compare Negated             | Update flags after $Rn + \text{shifter\_operand}$                    |
| 1100   | ORR      | Logical (inclusive) OR      | $Rd := Rn \text{ OR shifter\_operand}$                               |
| 1101   | MOV      | Move                        | $Rd := \text{shifter\_operand}$ (no first operand)                   |
| 1110   | BIC      | Bit Clear                   | $Rd := Rn \text{ AND NOT}(\text{shifter\_operand})$                  |
| 1111   | MVN      | Move Not                    | $Rd := \text{NOT shifter\_operand}$ (no first operand)               |

These 3 bits look like directly mappable ALU opcodes



# ALU in ARM7

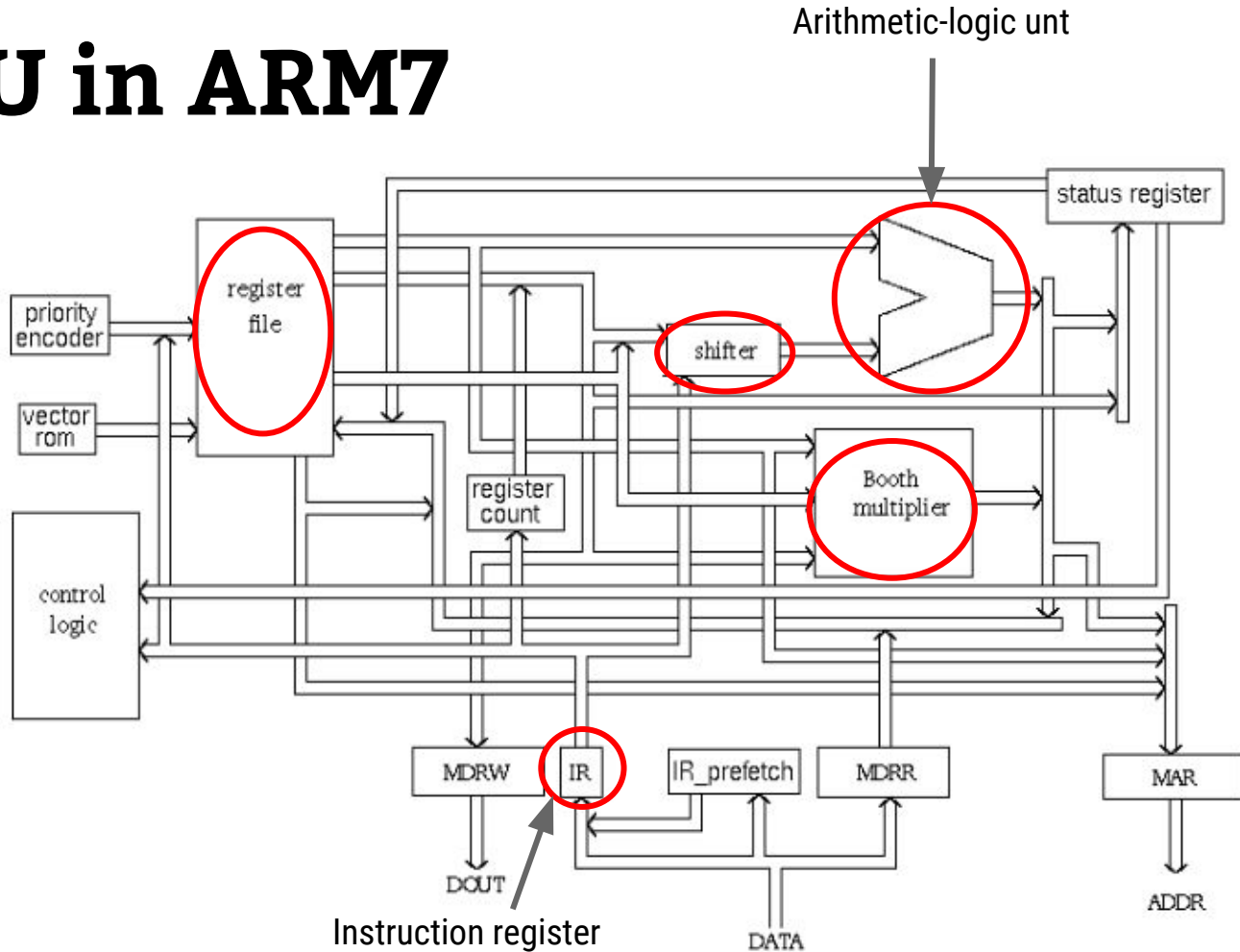

# Subtraction

Two's complement

# Negative numbers in binary

## UNSIGNED INTEGER

| Decimal | Bit Pattern |
|---------|-------------|
| 15      | 1111        |
| 14      | 1110        |
| 13      | 1101        |
| 12      | 1100        |
| 11      | 1011        |
| 10      | 1010        |
| 9       | 1001        |
| 8       | 1000        |
| 7       | 0111        |
| 6       | 0110        |
| 5       | 0101        |
| 4       | 0100        |
| 3       | 0011        |
| 2       | 0010        |
| 1       | 0001        |
| 0       | 0000        |

16 bit range:  
0 to 65,535

## OFFSET BINARY

| Decimal | Bit Pattern |
|---------|-------------|
| 8       | 1111        |
| 7       | 1110        |
| 6       | 1101        |
| 5       | 1100        |
| 4       | 1011        |
| 3       | 1010        |
| 2       | 1001        |
| 1       | 1000        |
| 0       | 0111        |
| -1      | 0110        |
| -2      | 0101        |
| -3      | 0100        |
| -4      | 0011        |
| -5      | 0010        |
| -6      | 0001        |
| -7      | 0000        |

16 bit range  
-32,767 to 32,768

## SIGN AND MAGNITUDE

| Decimal | Bit Pattern |
|---------|-------------|
| 7       | 0111        |
| 6       | 0110        |
| 5       | 0101        |
| 4       | 0100        |
| 3       | 0011        |
| 2       | 0010        |
| 1       | 0001        |
| 0       | 0000        |
| 0       | 1000        |
| -1      | 1001        |
| -2      | 1010        |
| -3      | 1011        |
| -4      | 1100        |
| -5      | 1101        |
| -6      | 1110        |
| -7      | 1111        |

16 bit range  
-32,767 to 32,767

## TWO'S COMPLEMENT

| Decimal | Bit Pattern |
|---------|-------------|
| 7       | 0111        |
| 6       | 0110        |
| 5       | 0101        |
| 4       | 0100        |
| 3       | 0011        |
| 2       | 0010        |
| 1       | 0001        |
| 0       | 0000        |
| -1      | 1111        |
| -2      | 1110        |
| -3      | 1101        |
| -4      | 1100        |
| -5      | 1011        |
| -6      | 1010        |
| -7      | 1001        |
| -8      | 1000        |

16 bit range  
-32,768 to 32,767


# Binary subtraction

- Addition of negative number
- Minuend is added to inverted bits of subtrahend and 1 (due to offset)

| Decimal     | Twos Complement |            |
|-------------|-----------------|------------|
| 17          | 00010001        | Minuend    |
| <u>10</u> - | 11110101        | Subtrahend |
|             | <u>1</u>        | + Plus 1   |
|             | (1)11100010     | Carry      |
| <u>7</u>    | <u>00000111</u> | Answer     |
|             | ↓               |            |
|             | Discarded       |            |
 
# Subtraction in hardware

subtraction flag from the  
opcode inverts bits of  
second operand and sets  
carry in to 1



# Binary multiplication

- Implemented with
  - AND operation
  - Binary addition
- Booth's multiplier
  - Group bits
  - Precalculate addends

## BINARY MULTIPLICATION

$$\begin{array}{r} 1101 \quad (13) \\ \times 1011 \quad (11) \\ \hline 1011 \\ + 0000 \\ 1011 \\ 1011 \\ \hline 10001111 \quad (143) \end{array}$$

Binary multiplication is even easier than decimal, because we have either multiplication by 1 or by 0 in the intermediate sums.

# Beyond multiplication



- There aren't many interesting operations that can be performed on integers
- Most mathematical functions (div, sqrt, exp, sin, cos, tan) are approximations
- Possible implementations
  - Lookup table
  - Polynomial approximation
  - CORDIC

# Old school hacks to get stuff faster

- Precalculate results of certain slow operations when the program is started
- Place the results in a lookup table (array)
- When looking up value find nearest two results
- Interpolate the result from two nearest results
- For sine, cosine use single lookup table for first 90 degrees only


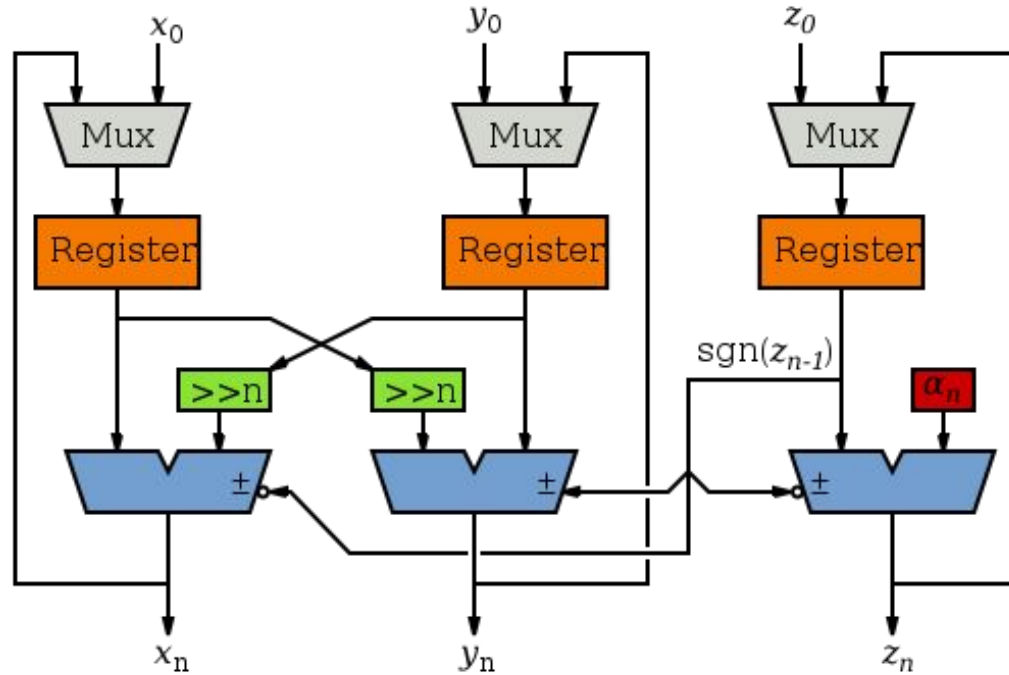 
# Coordinate Rotation Digital Computer (CORDIC)



# Fast $\frac{1}{\sqrt{x}}$ in Quake 3


```
float Q_rsqrt( float number ) {  
    long i;  
    float x2, y;  
    const float threehalfs = 1.5F;  
    x2 = number * 0.5F;  
    y = number;  
    i = * ( long * ) &y;          // evil floating point bit level hacking  
    i = 0x5f3759df - ( i >> 1 ); // what the fuck?  
    y = * ( float * ) &i;  
    y = y * ( threehalfs - ( x2 * y * y ) );  
    return y;  
}
```

# Assignment


Adder/ALU
 
# Assignment

- Use 7400 chips to implement carry ripple adder
- Get up to 4 points depending on how many FA-s you can wire
- 2 extra points for adding toggleable subtracting



# Full adder

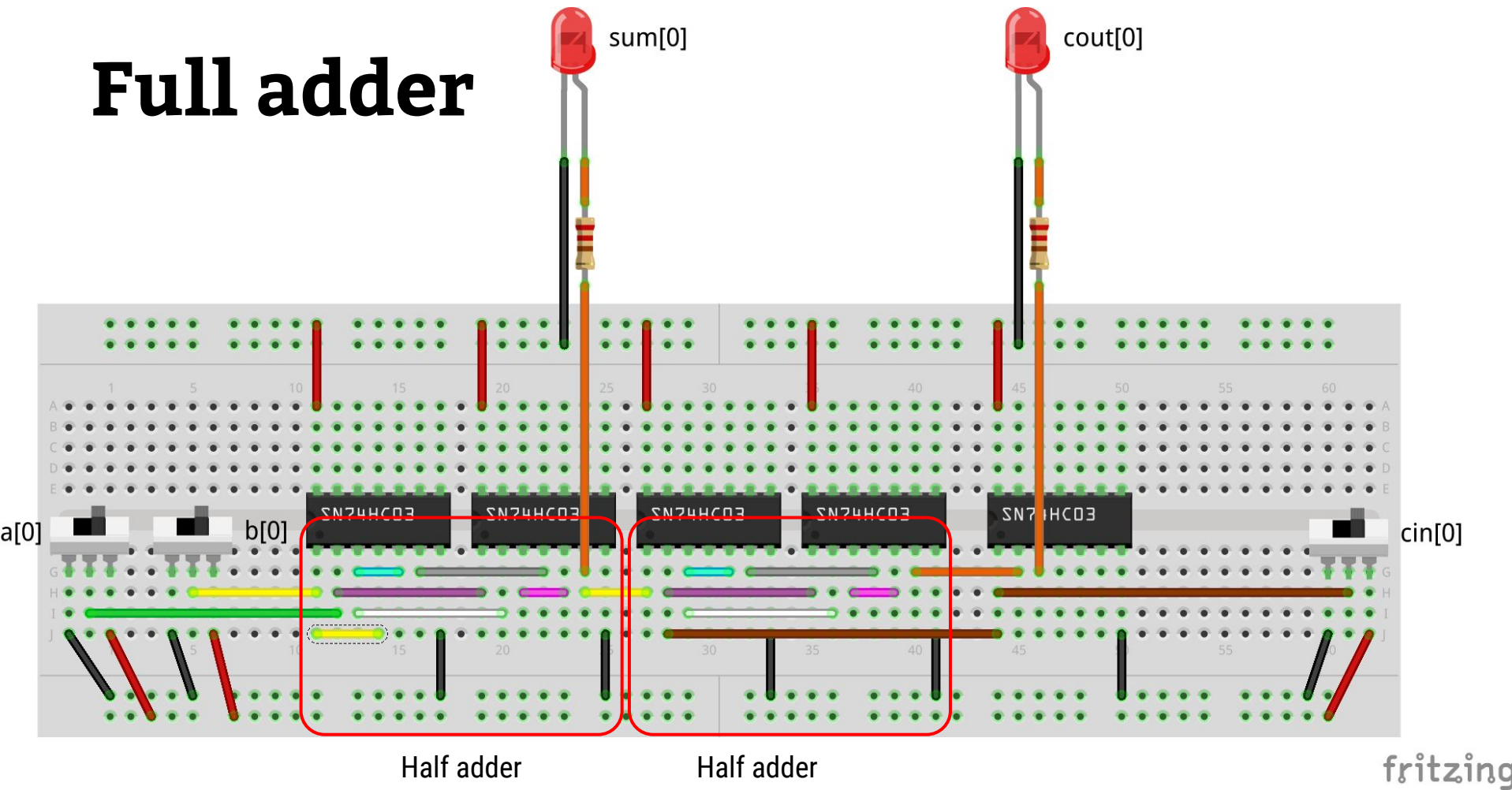

# Some tips

- One breadboard (5 chips) should be enough to implement 2-bit adder
- Another board (+4 chips) is required to implement 4-bit adder
- Add another board (+4 chips) to implement subtractor logic
- Use Arduino to run a testbench against the circuit

# Karnaugh map for full adder

- Determine inputs
- Determine outputs
- Derive truth table for each output bit
- Use Karnaugh map to derive Boole formula
- $\text{Sum} = (!A \text{ AND } !B \text{ AND } C) \text{ OR } (!A \text{ AND } B \text{ AND } !C) \dots$
- $\text{Cout} = (B \text{ AND } C_{in}) \text{ OR } (A \text{ AND } C_{in}) \text{ OR } (A \text{ AND } B)$

